


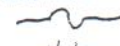
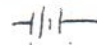



YOUR NAME \_\_\_\_\_

MATCH THE BEST ANSWER AND PLACE THE LETTER ON YOUR ANSWER SHEET

\*\* \*\*

- 1 \_\_\_ Volt
- 2 \_\_\_ Amp
- 3 \_\_\_ Ohm
- 4 \_\_\_  $V=A \times D$
- 5 \_\_\_ Atom
- 6 \_\_\_ Electron
- 7 \_\_\_ Conductor
- 8 \_\_\_ Insulator
- 9 \_\_\_ Copper
- 10 \_\_\_ Rubber
- 11 \_\_\_ Fuse
- 12 \_\_\_ Circuit Breaker
- 13 \_\_\_ Fusible link
- 14 \_\_\_ Bulb
- 15 \_\_\_ Fuse
- 16 \_\_\_ Ground
- 17 \_\_\_ Switch
- 18 \_\_\_ Battery
- 19 \_\_\_ Resistor
- 20 \_\_\_ Ground

*Symbols*

- A. 
- B. Unit of electrical resistance
- C. An electrical protective device.
- D. Prevents electricity from flowing
- E. These in combination are used to form elements.
- F. It takes many millions of these to form an amp.
- G. An electrical protective device.
- H. A common insulator for electricity.
- I. 
- J. 
- K. Electricity will flow through this.
- L. 
- M. An electrical protective device.
- N. Unit of electrical flow
- O. Ohms law
- P. Unit of electrical pressure.
- Q. 
- R. 
- S. A common conductor of electricity.
- T. 